## The All-wave "Round the World" Two



HEN analysed, most short-wave sets will be found to consist of a detector-valve in one of its most simple forms, followed by one or two stages of transformer coupling. Simplicity is the keynote of efficiency, and

although stunt circuits have been published, they have not held their own against the very simplest. Either they have been unstable in operation and difficult to tune, or inefficient in

general performance.

Referring to the theoretical diagram, it can be seen to consist of a single detector with a single stage of audio amplification, to which another stage can be easily added. The audio-frequency path from the detector-valve will be seen to be taken from the opposite end of the reaction coil to the usual method, as this was found to give smoother reaction control with less body capacity. The dotted line showing the earth connection was found to be unnecessary in a number of cases, sufficient capacity to earth being produced by the various battery cables,

#### Mounting the Components.

AN ebonite panel, 12in. long by 6in. high, will give ample room for well spacing, and the baseboard measuring at least 9in. from back to front will allow the coils to be placed at a distance from the metal plates of the condenser. It is small points like this which make all the difference, and an overcrowded receiver suffers from the disadvantage that it is extremely sharp in tuning, often making a station impossible to retain when the hand is taken from the controls.

Screw the panel to the front edge of one of smallest capacity being on the struction will be given in detail. left. Choose condensers having low loss

### A Revision of One of Our Most Popular Receivers

Just about twelve months ago "Pentode" described the "Round the World" Two, and he claimed that it was reliable and did not suffer from Results the usual drawbacks associated with short-wave receivers. have shown this to be a very modest claim, for the set has been constructed by hundreds of radio enthusiasts and we have received numerous congratulatory letters. Only twice has there been something serious to hamper the constructor, and of these one did not follow the instructions. So many have called upon our stocks of the original number of the "Radio Record" in which the receiver was described, that our supplies have long since been exhausted. The numerous demands for a redescription have prompted us to redescribe the set and incorporate a few improvements, including broadcast coils and an extra stage.

are that many unexplained noises will and allow of a smaller tuning condenaccompany every movement of the ser, making for ease of tuning. tuning controls.

In the centre is mounted the detector rheostat, the resistance of which is PROCURE a length of cardboard chosen to suit the nationlar valve chosen to suit the particular valve

#### Data for the Coils.

tubing of 3in. outside diameter, used. If of .25 ampere consumption, a and cut into three longitudinal sections. rheostat of 15 ohms will be sutaible, The tube will need to be about 9 or

#### but if of .1 amp. consumption (which 10 inches long in order to possess a

#### Components for "Round-the-World" Two

- 1 Variable condenser (low loss .0002 m.f.d.).
- Variable condenser, .00035 m.f.d. 2 Fixed condensers, .0002 with leak, 7 meg. and .0003 m.f.d.
- condenser. 2 Anti-microphonic valve sockets.
- 1 15-30 ohm Rheostat.
- 1 Audio transformer (1-5 ratio).
- 2 Vernier dials.
- 1 Midget neutralising condenser. Panel and baseboard.
- 1 doz. Terminals.
- 18 gauge enamelled or tinned copper wire.
- 1 Amperite.
- 44 Valve pins and sockets.
- Ebonite strips, etc.

#### 

we recommend) then a 30 ohm rheostat good grip while winding the coil. Now will give better control. On the right fasten the three sections together with the baseboard, using two brackets if no hand bottom corner is mounted the adhesive tape or gummed paper, and cabinet is to be used. The two con-speaker or 'phone jack. As the coils wrap round two or three turns of strips, thus holding the wire firmly, densers are mounted on the front, the play such an important part, their con- brown paper. This makes an ideal and keeping a constant spacing between

features, and if no pigtail connection is range of from 10 to 70 metres, a set provided between the moving plates of coils will have to be made, consistand the terminal, solder on a small ing of 4, 5, 6, 8 and 12 turns. This may and the terminal, solder on a small ing of 2, 5, 8 and 12 turns. This may length of flexible stranded wire. With seem a large number of separate coils, making a neat job is to fasten one end coils, each having the following numout this positive connection, the changes but they also cover the reaction coils. out this positive connection, the chances but they also cover the reaction coils,

former on which to wind any self- turns. When thoroughly dry dismantle To obtain a complete wavelength supporting coil. The wire used is 18 the cardboard former, taking care not S.W.G. tinned or enamelled copper, to damage the coil. We now have a and a length of about 32 feet will be self-supporting, low loss coil, which necessary. Perhaps the easiest way of will have to be divided into smaller

the diameter of the wire, but preferably


slightly larger. One-eighth inch spac-

tremely efficient inductance.

It should have been mentioned that before winding on this wire lay three strips of celluloid along the former, equidistant, winding the wire round the whole. The reason for this will be apparent presently.

A full forty turns in one length is required, which is cut up presently. After making the remaining end tight in a similar way to the first, end, proceed to unwind the spacing string: &

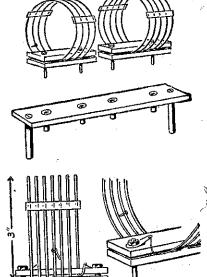Fairly thick celluloid cement is us to paint on, along each of the celluloid



# DIALS Plain and Vernier for All Types of Sets

#### NOTE OUR PRICES:


2 and 4in. Plain Black Bakelite 1/- each Wavemaster 24 to 1 Vernier 3/6 each Bisby De Luxe Vernier Level. 5/6 each Ormond SW. Vernier-

We always carry a large range of Dials—the quality is the best-and the Prices Low.

Send for our 40-page List.

#### B. SCOTT LTD.

BOX 395, CHRISTCHURCH.

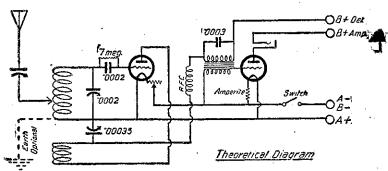

#### Mounting the Coils.

and sockets will be needed. Four quirement, but each coil having two gether. This string should be at least contacts will necessitate the use of 10 valve pins. Choose ones having about lin, of tapped metal at one end, and if ing between wires results in an ex- no shoulder is provided, two nuts to each pin will be required.

